

EE140 LAB1 report

Shengxi Liang

PART1


Hand-Calculation: 1.A

1. A. $I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$ $I_{D1} = I_{D2}$

$R_d = 0$. $V_{B1} = 1.1V$. $V_{GS1} = 1.1V$.

$I_D = 40.5 \mu A$.

$g_{m1} = 2.7 \times 10^{-4} S$

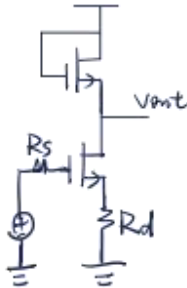

$g_{m2} = \mu C_{ox} \frac{W_2}{L_2} (V_{GS} - V_{TH}) = \frac{2I_D}{V_{GS} - V_{TH}} = \sqrt{2\mu C_{ox} \frac{W_2}{L_2} I_D} = 2.8 \times 10^{-5} S \Rightarrow \frac{1}{g_{m2}} = 3.5 \times 10^4$


$r_{o1} = r_{o2} = \frac{1}{\lambda I_D} = 2.47 \times 10^6 \Omega$

$g_{m2} = 2.8 \times 10^{-4} S$.

$r_{out} = r_{o1} \parallel \frac{1}{g_{m2}} = 2.8 \times 10^4 \Omega$.

$g_{m1} = \sqrt{2\mu C_{ox} \frac{W_1}{L_1} I_D} = 2.7 \times 10^{-4} S$.

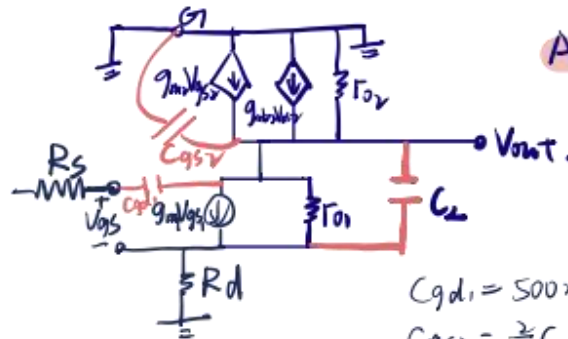$A_v = \frac{g_{m1}}{g_{m1} + g_{m2}} = 7.8$.



$C_{ox1} = \frac{\epsilon_r \epsilon_0 A}{t_{ox}} = \frac{W \cdot L \cdot \epsilon}{t_{ox}} = 4.3 \times 10^{-10} F$

$C_{ox2} = \frac{\epsilon_r \epsilon_0 A}{t_{ox}} = \frac{W \cdot L \cdot \epsilon}{t_{ox}} = 1.55 \times 10^{-12} F$.

$C_{gd1} = 500 \times 10^{-12} \times 50 \times 10^{-6} = 2.5 \times 10^{-14} F$.

$C_{gs2} = \frac{2}{3} C_{ox2} = 1.5 \times \frac{2}{3} \times 10^{-12} = 1.03 \times 10^{-12} F$

$\tau_1 = r_{out} C_L = 2.5 \times 10^{-12} \times 2.8 \times 10^4 = 70 ns$

$\tau_2 = r_{out1} C_{gd1} = \left[(r_{o1} + R_s) \left(1 - \frac{r_{o1}}{1 + g_{m1} R_d} \right) + r_{o1} \parallel \frac{r_{o2}}{1 + g_{m2} R_d} \cdot R_s \right] C_{gd1}$


= very small.

$\tau_3 = r_{out2} C_{gs2} = \left(r_{o2} \parallel \frac{1}{g_{m2} + g_{m1}} \right) C_{gs2}$

$= 28.8 \times 10^3 \times 1.03 \times 10^{-12} F = 70 ns$.

$BW = \frac{1}{\tau_1 + \tau_2 + \tau_3} = \frac{1}{2\pi \cdot 100 \times 10^{-9}} = 1.6 MHz$.

Simulation: 1.A

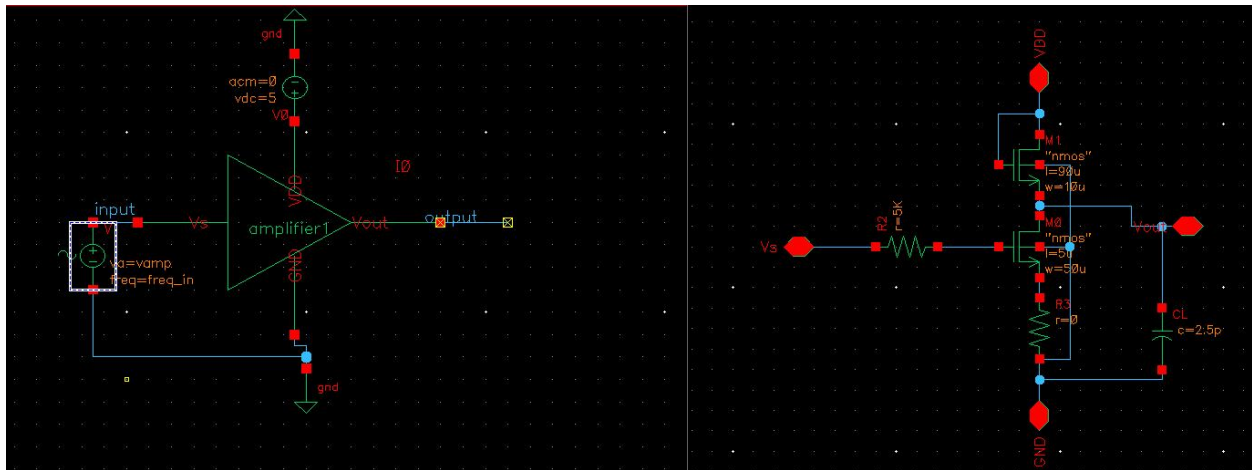

vout/vs & Bandwidth

Outputs				
Name/Signal/Expr	Value	Plot	Save	Save Options
1 out_AC	wave	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
2 midband_gain	7.716	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
3 3dB_bandwidth	1.422M	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	

Plot after simulation: Auto Plotting mode: Replace


Rout

Outputs				
Name/Signal/Expr	Value	Plot	Save	Save Options
3 3dB_bandwidth		<input type="checkbox"/>	<input checked="" type="checkbox"/>	
4 rout	28.46 K	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
5 db_out		<input type="checkbox"/>	<input type="checkbox"/>	


Plot after simulation: Auto Plotting mode: Replace

Status: Ready T=27 C Simulator: spectre State: state 1

Magnitude of gain

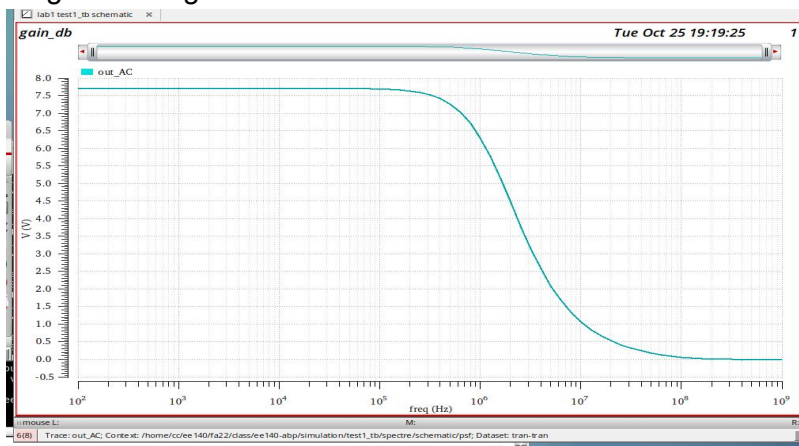


Maximum output voltage swing

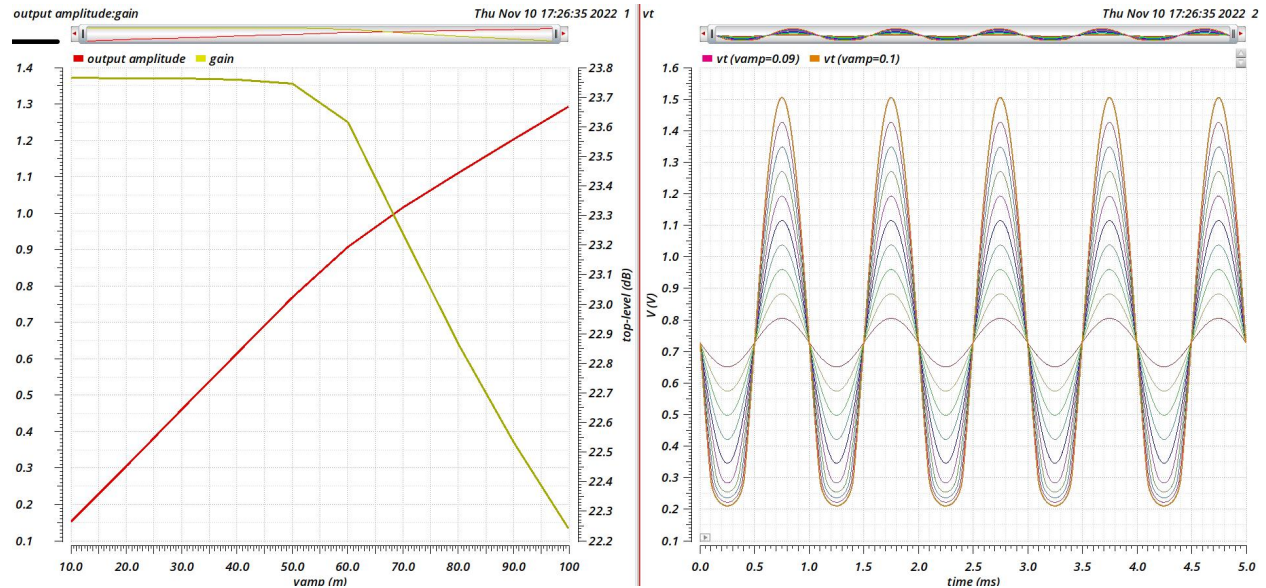

Output swing: $1.5V - 0.2V = 1.3V$

In this part, we found that the differences of hand-calculation and simulation is not very noticeable (table 1), but it can't be ignored. Due to the fact that in the process of hand calculation, we ignored lateral diffusion and sometimes we ignored body effect, so the R_{out} and mid-band gain from hand-calculation and simulation are different in a small degree. Especially for bandwidth, we learned that in the process of hand-calculation, we used the asymptotic approximation technique, so it has a very obvious difference.

Hand-calculation: 1.B

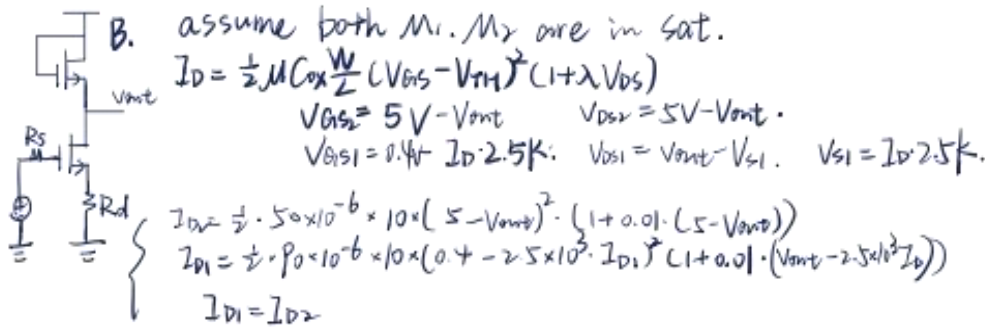

$$\Rightarrow I_D = 40.3 \mu A, \quad V_{out} = 1.36 V, \quad V_{S1} = I_D \cdot R_d = 0.1 V$$

$$V_{DS1} > V_{GS1} - V_{TH1} \quad \checkmark \quad V_{DS2} > V_{GS2} - V_{TH2} \quad \checkmark$$

\therefore both in sat is correct.

$$r_o = r_{o1} = r_{o2} = \frac{1}{\lambda I_D} = \frac{1}{0.01 \times 40.3 \times 10^{-6}} = 2.48 M\Omega$$


$$g_{m1} = \frac{2I_D}{2V_{GS1}} = \frac{2I_D}{V_{out} - V_{S1} - V_{TH1}} = 175 \mu S, \quad g_{m2} = \frac{2I_D}{2V_{GS2}} = \frac{2I_D}{5V - V_{out} - V_{TH2}} = 28.4 \mu S$$

$$g_{mb1} = \frac{g_{m1}}{2 \sqrt{2\phi_F + V_{S1}}} = \frac{0.8 \times 175 \times 10^{-6}}{2 \sqrt{2 \times 0.7 + 1.2}} = 4.34 \times 10^{-5} S, \quad g_{mb2} = \frac{g_{m2}}{2 \sqrt{2\phi_F + V_{S2}}} = \frac{0.8 \times 28.4 \times 10^{-6}}{2 \sqrt{2 \times 0.7 + 5}} = 4.5 \times 10^{-6} S$$

$$R_{out} = \left[\frac{1}{g_{m1} + g_{mb2}} \parallel r_{o2} \right] \parallel [r_{o1} + R_d + r_{o1} R_d (g_{mb1} + g_{m1})]$$

$$= 30.4 K \parallel 3.74 \times 10^6 \Omega \approx 30.4 K\Omega$$
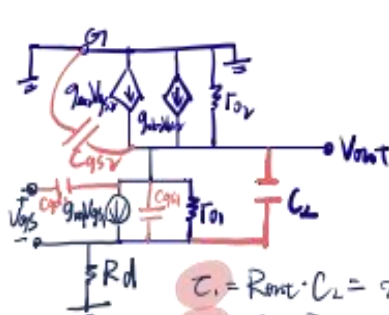
$$A_v = -G_m \cdot R_{out}, \quad G_m = \frac{i_{sc}}{V_{in}} = \frac{g_{m1}}{R_d \cdot (g_{m1} + \frac{1}{r_{o1}} + \frac{1}{R_d})} = 185 \mu S, \quad A_v = -5.6$$



$$C_{ox1} = \frac{\epsilon_r \epsilon_0 A}{t_{ox}} = \frac{W \cdot L \cdot \epsilon}{t_{ox}} = 4.3 \times 10^{-10} F$$

$$C_{ox2} = \frac{\epsilon_r \epsilon_0 A}{t_{ox}} = \frac{W \cdot L \cdot \epsilon}{t_{ox}} = 1.55 \times 10^{-12} F$$

$$C_{gd1} = 500 \times 10^{-12} \times 50 \times 10^{-6} = 2.5 \times 10^{-14} F$$

$$C_{gs2} = \frac{2}{3} C_{ox2} = 1.55 \times \frac{2}{3} \times 10^{-12} = 1.03 \times 10^{-12} F$$

$$C_{gs1} = \frac{2}{3} C_{ox1} = 2.87 \times 10^{-10} F$$

$$C_1 = R_{out} \cdot C_2 = 2.5 pF \cdot 30.4 K\Omega = 7.6 \times 10^{-8} s$$

$$C_2 = C_{gs2} R_2 = 1 pF \cdot 30.4 K\Omega = 3.04 \times 10^{-8} s$$

$$i_t = g_{m1} V_{in} - \frac{V_{out}}{r_{o2}} = \frac{V_{out}}{r_{o1}} + \frac{V_{out}}{r_{o1} \left(\frac{1}{R_d} + g_{mb1} \right)}$$

$$\Rightarrow R_2 = \frac{V_{out}}{i_t} = \frac{1}{g_{m1} + \frac{1}{r_{o1}} + \frac{1}{r_{o2}} + \frac{1}{r_{o1} (g_{mb1} + \frac{1}{R_d})}} = 25.2 K\Omega$$

$$Z_3 = C_{gd1} \cdot R_{gd1} = \text{very small.}$$

$$Z_4 = C_{gs1} \cdot R_{gs1} = 2.87 \times 10^{-10} \times 1.5 \times 10^3 = 4.3 \times 10^{-7} \text{ s.}$$


$$i_v + g_{mb1}(-V_{t1}) + \frac{V_{out}}{F_{o1}} = g_{m2} \cdot V_{out} + \frac{V_{out}}{F_{o2}}$$

$$\Rightarrow R_{gs1} = \frac{V_P}{i_v} = 1.5 \text{ k}\Omega.$$

$$V_{out} = \frac{V_P}{R_d(g_{m2} + \frac{1}{F_{o2}})}$$

$$BW = \frac{1}{(Z_1 + Z_2 + Z_3 + Z_4)} = 1.443 \text{ MHz.}$$

Simulation : 1.B

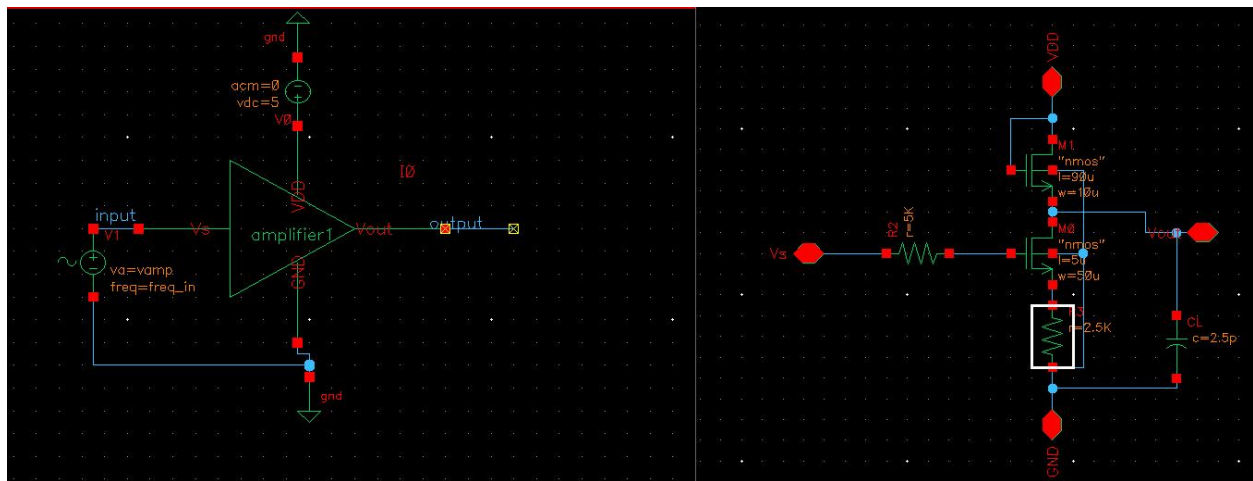

vout/vs & Bandwidth

ADE L (1) - lab1 test1_tb schematic

Launch Session Setup Analyses Variables Outputs Simulation Results Tools Help

Design Variables

Name	Value
1 vb1	1.2V
2 v amp	1V

Analyses

Type	Enable	Arguments
1 ac	<input checked="" type="checkbox"/>	100 1G 10 Logarithmic Points Per Decade Start-Stop
2 dc	<input type="checkbox"/>	-100m 100m Automatic Start-Stop

Outputs

Name/Signal/Expr	Value	Plot	Save	Save Options
1 out_AC	wave	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
2 midband_gain	4.175	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
3 3dB_bandwidth	1.297M	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
4 rout		<input type="checkbox"/>	<input type="checkbox"/>	


Rout

	Name/Signal/Expr	Value	Plot	Save	Save Options
1	out_AC	wave	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
2	midband_gain		<input type="checkbox"/>	<input type="checkbox"/>	
3	3dB_bandwidth		<input type="checkbox"/>	<input type="checkbox"/>	
4	rout	31.47K	<input checked="" type="checkbox"/>	<input type="checkbox"/>	


Plot after simulation: Auto Plotting mode: Replace

Status: Ready | T=27 C | Simulator: spectre | State: state4

Magnitude of gain

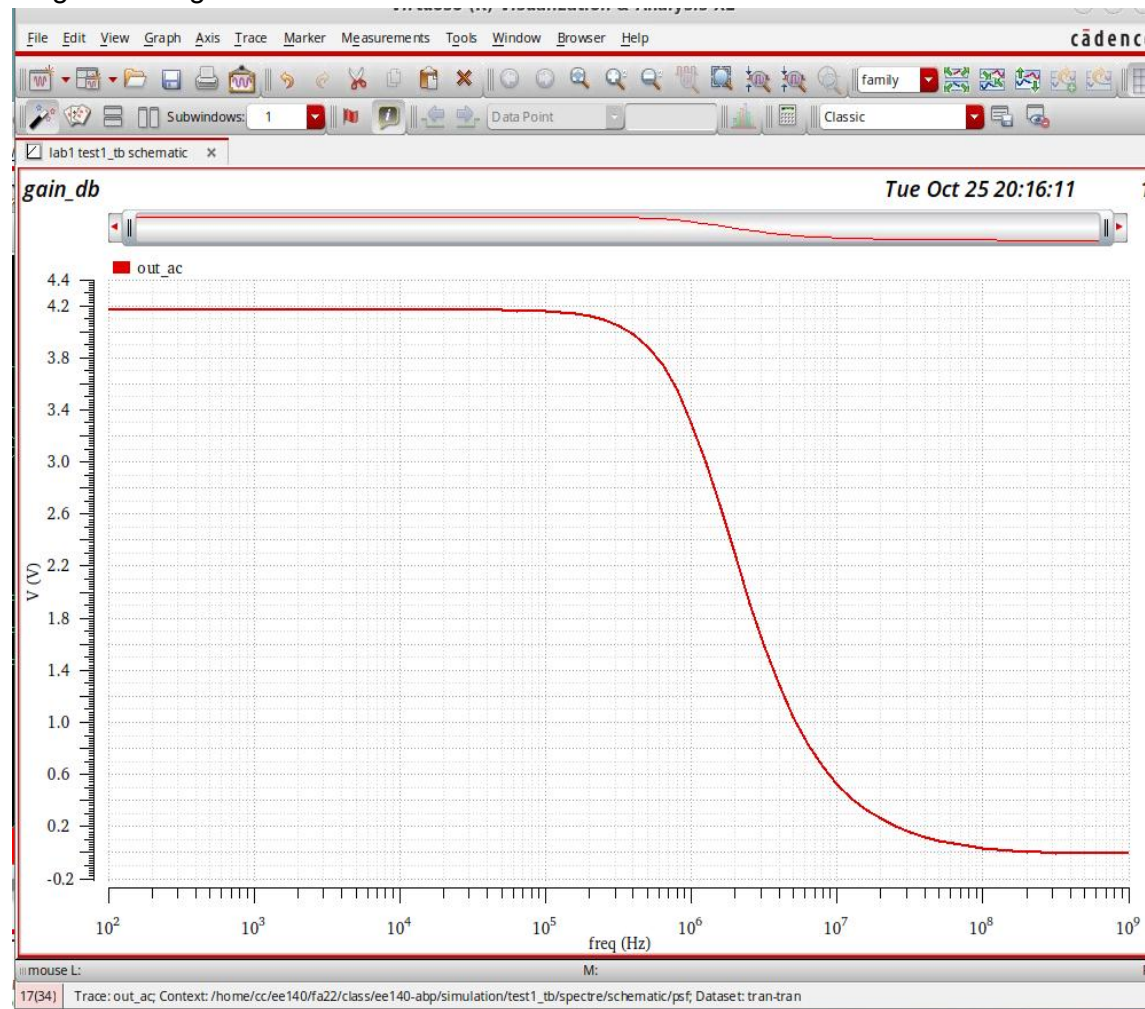

Maximum output voltage swing

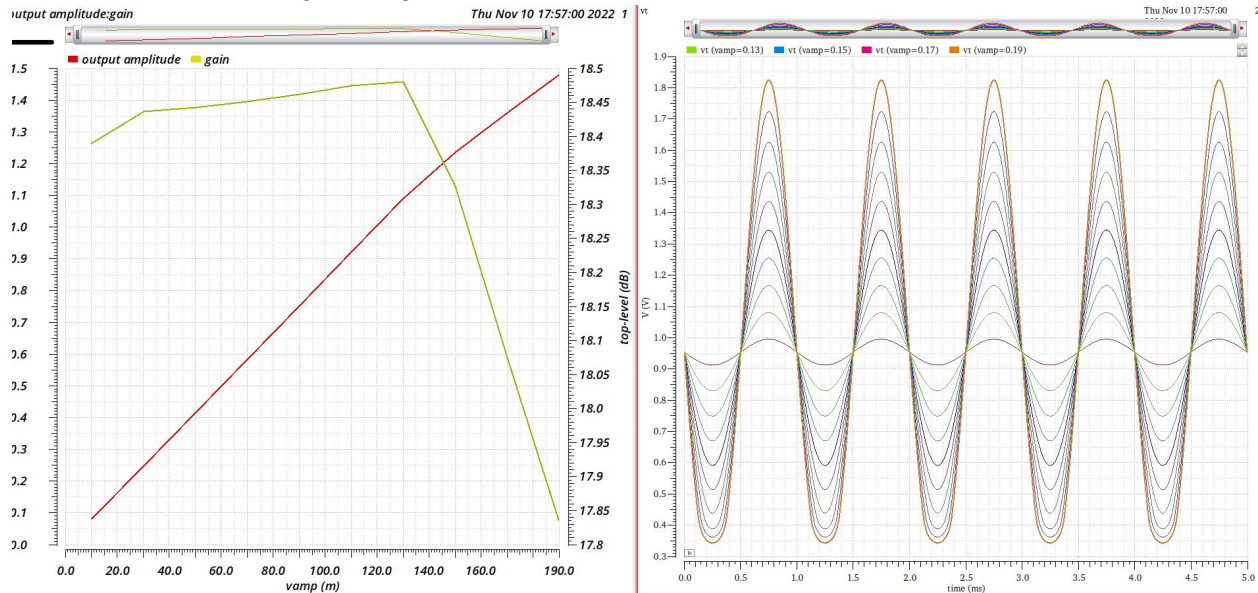

When $v_{amp}=0.15V$, we got the maximum output swing: $1.82V - 0.35V = 1.47V$

In part B, we found that the differences of hand-calculation and simulation is much more obvious than part A (table 1), it is because we have $R_d=2.5k\Omega$, not 0, the mid-band gain is influenced a lot.

Due to the fact that in the process of hand calculation, we ignored lateral diffusion and sometimes we ignored body effect, the R_{out} from hand-calculation and simulation are different in a small degree.

Additionally, for bandwidth, we learned that in the process of hand-calculation, we used the asymptotic approximation technique, so it has a very obvious difference.

	1A calculation	1A simulation	1B calculation	1B simulation
R_{out}	28.1k Ω	28.46k Ω	30.4k Ω	31.47k Ω
BW	1.6MHz	1.422MHz	1.443MHz	1.297MHz
Mid-band gain	7.8	7.7	5.6	4.175

Table 1 list of relevant perform parameters

From A to B, we got almost same bandwidth, but midband gain is lower.

PART2:

Parameter	Specification – EE140	Specification – EE240A
Midband gain	$\geq 120 \text{ V/V}$	$\geq 140 \text{ V/V}$
3 dB cutoff frequency (bandwidth)	$\geq 180 \text{ kHz}$	$\geq 200 \text{ kHz}$
Output voltage swing	$\geq 3 \text{ V}_{pp}$	
Load capacitance	2.5 pF	
Source resistance	$5 \text{ k}\Omega$	
Supply voltage	$V_{DD} = 5 \text{ V}, V_{SS} = \text{Ground} = 0 \text{ V}$	

Hand-calculation 2:

In the process of doing hand-writing, firstly I choose the specification of my design. And I try to let every transistor is in saturation.

From these specs, I can get g_m first. Then we find the R_{out} of this circuit as function of I_D . Due to the fact that g_m can be calculate with ΔV_1 and I_D , we use an approximation to let $G_m = g_{m1}$.

Now we can get the function of mid-band gain, which is only depends on ΔV_1 , rather than I_D . With ΔV_1 , g_m , we are able to calculate I_D .

As I have choose the specs of design. We got the boundary of ΔV_1 and ΔV_2 from output swing.

From the boundary of ΔV_1 and ΔV_2 , we choose a pair of value to calculate R_{out} , mid-band gain as well as bandwidth until they meet requirements.

Now we got everything we need to calculation the right W_1 , W_2 .

As we are suggested to use correct mirror to bias M_2 , we do calculation to find the width of another pmos, and found the correct I_{bias} .

sat (even mV change)

$$(\mu_{Cox})_n = 90 \mu A/V^2 \quad (\mu_{Cox})_p = 30 \mu A/V^2$$

2.

V_{B1}

(current mirror)

V_{B2}

$$\frac{W_1}{L_1} = \frac{W_1}{5 \mu m}$$

$$\frac{W_2}{L_2} = \frac{W_2}{5 \mu m}$$

hint from instructions:

$$|V_{GS}| > 1V$$

$$g_m = \mu_{Cox} \frac{W}{L} (V_{GS} - V_{TH}) = \frac{2I_D}{V_{GS} - V_{TH}} = \sqrt{2\mu_{Cox} \frac{W}{L} I_D}$$

$$r_o = \frac{1}{\lambda I_D}$$

$$I_D = \frac{1}{2} \mu_{Cox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$


$$V_{GS1} = V_{DD} - V_{out}$$

$$V_{GS2} = V_{out}$$

$$V_{GS1} = V_{B2} - V_{out}$$

$$V_{GS2} = V_{B1}$$
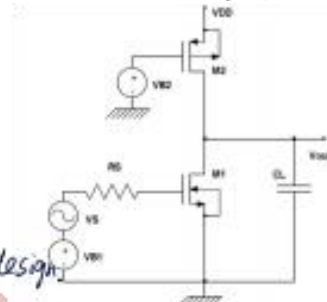
$$\lambda_1 = 0.01 \quad \lambda_2 = 0.02$$



To begin with, we choose the specifications of design:

① Midband-gain: $150 V/V$. ② bandwidth: $250 kHz$

③ outputs swing = $V_{DD} - \Delta V_2 - \Delta V_1 \geq 3V_{pp} \Rightarrow \Delta V_1 + \Delta V_2 \leq 2V$

other constraints: ① $L = 5 \mu m$. ② all in saturation. ③ $|V_{GS}| \geq 1V$

start calculation:

$$A_{f_{BW}} = g_m R_{out} = \frac{1}{2\pi R_{out} C_L}$$

$$\therefore g_m = 2\pi \cdot C_L \cdot A \cdot f_{BW} = 2\pi \cdot 2.5 \times 10^{-12} \cdot 150 \cdot 250 \times 10^3 = 589 \mu S$$

$$R_{out} = r_{o1} \parallel r_{o2} = \frac{1}{0.01 I_D} \parallel \frac{1}{0.02 I_D} = \frac{1}{0.03 I_D}$$

$$A = g_m R_{out} \geq 150 \quad \frac{2I_D}{\Delta V_1} \cdot \frac{1}{0.03 I_D} = \frac{200}{3\Delta V_1} \geq 150 \Rightarrow \Delta V_1 \leq 0.44 V$$

$$\Delta V_1 + \Delta V_2 \leq 2V \Rightarrow \Delta V_2 \leq 1.56 V$$

$$\text{if we choose } \Delta V_1 = 0.39 V, I_D = \frac{\Delta V_1 \cdot g_m}{2} = 1.17 \times 10^{-4} A$$

$$\Rightarrow r_{o1} = 852 K\Omega \quad r_{o2} = 426 K\Omega$$

$$R_{out} = 284 K\Omega$$

$$\Rightarrow A_v = g_m R_{out} = 167$$

$$BW = \frac{1}{2\pi R_{out} \cdot C_L} = 224 kHz$$

These certificate that.
 \Rightarrow we can choose
 $\Delta V_1 = 0.39 V$ $V_{B1} = 1.19 V$
 $\Delta V_2 = 1.56 V$ $V_{B2} = 2.25 V$

$$W_1 = \frac{2I_D L}{(\mu C_{ox})_n \Delta V_1^2} = \frac{2 \times 117 \times 50 \times 10^{-6}}{90 \times 0.39^2} = 80 \mu m$$

$$W_2 = \frac{2I_D L}{(\mu C_{ox})_p \Delta V_2^2} = \frac{2 \times 117 \times 50 \times 10^{-6}}{30 \times 1.45^2} = 24.4 \mu m$$

current mirror. $V_{D2} = V_{D3} = 2.25V$, $V_{G2} = V_{G3}$

$$\frac{I_D}{I_{bias}} = \frac{\left(\frac{W}{L}\right)_2 (1 + \lambda_p V_{DS2})}{\left(\frac{W}{L}\right)_3 (1 + \lambda_p (V_{DS3} - V_{DS2}))} = 1 \Rightarrow \left(\frac{W}{L}\right)_3 \approx \left(\frac{W}{L}\right)_2 \quad W_3 = 24.4 \mu m$$

when we use this W_3 to build a current mirror, we found that specs is what we want.


$$I_{bias} = I_{D1} = I_{D2}$$

$$I_{D1} = \frac{1}{2} (\mu C_{ox})_n \Delta V_1^2 \cdot (1 + \lambda_n V_{DS1})$$

$$\Rightarrow I_{bias} = \frac{1}{2} \cdot 70 \cdot 10^{-6} \cdot 0.39^2 \cdot (1 + 0.01 \cdot 3) = 1.17 \times 10^{-4} A.$$


Simulation 2:

When we use explicit voltage:

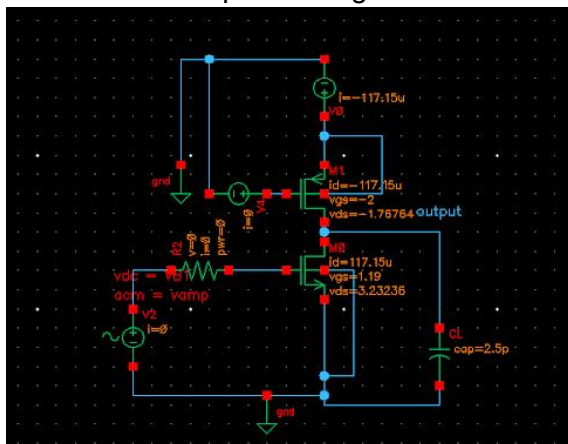

Outputs					
Name/Signal/Expr	Value	Plot	Save	Save Options	
1 3dB_bandwidth	326.624K	<input checked="" type="checkbox"/>	<input type="checkbox"/>		
2 midband_gain	103.614	<input checked="" type="checkbox"/>	<input type="checkbox"/>		
3 out_swing	3.23236	<input checked="" type="checkbox"/>	<input type="checkbox"/>		
4 out_AC	wave	<input checked="" type="checkbox"/>	<input type="checkbox"/>		
5 db_out	wave	<input checked="" type="checkbox"/>	<input type="checkbox"/>		
6 output	wave	<input checked="" type="checkbox"/>	<input type="checkbox"/>		

When we use current mirror:

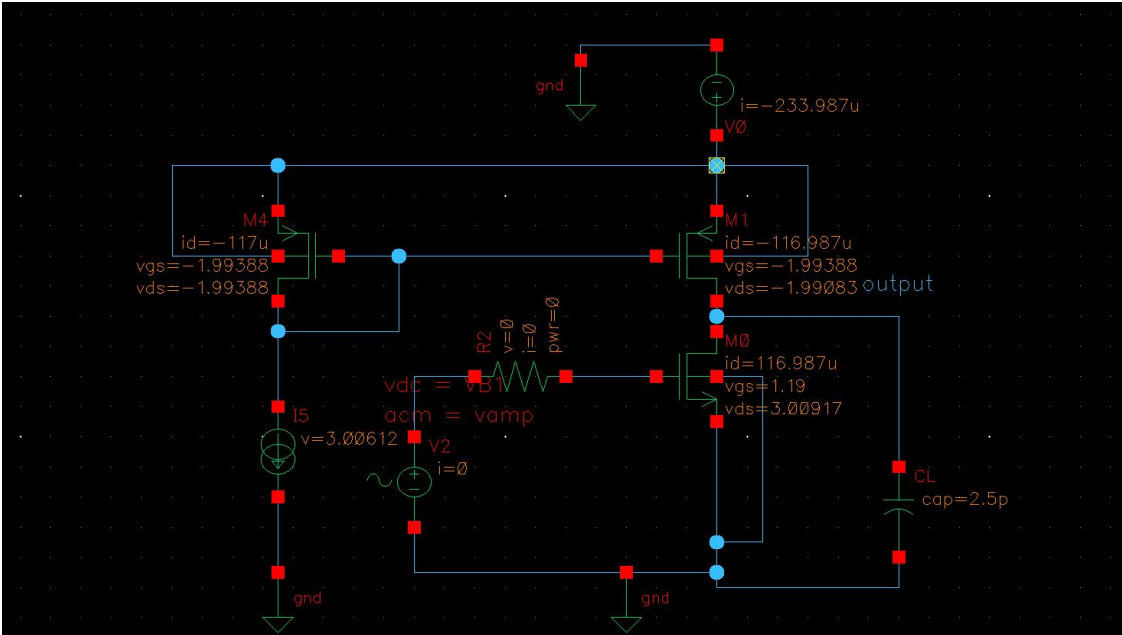

Outputs					
Name/Signal/Expr	Value	Plot	Save	Save Options	
1 3dB_bandwidth	290.673K	<input checked="" type="checkbox"/>	<input type="checkbox"/>		
2 midband_gain	115.873	<input checked="" type="checkbox"/>	<input type="checkbox"/>		
3 out_swing	3.00917	<input checked="" type="checkbox"/>	<input type="checkbox"/>		
4 out_AC	wave	<input checked="" type="checkbox"/>	<input type="checkbox"/>		
5 db_out	wave	<input checked="" type="checkbox"/>	<input type="checkbox"/>		
6 output	wave	<input checked="" type="checkbox"/>	<input type="checkbox"/>		

	Hand-calculation	Simulation with current mirror	Simulation with explicit voltage bias
bandwidth	224kHz	290.673kHz	326.624kHz
Midband gain	120	115.873	103.614
Out swing	3.15	3.01	3.23

Now we can explain some questions of our designs.

1. We found that using explicit voltage sources to bias amplifiers is not good practice, it is because as we need different voltage to bias transistor, it is not very realistic that a piece of IC connected to many different power supplies. Additionally, explicit voltage sources introduce noises to the system.
2. As we rework the biasing network and simulate the gain and bandwidth of our amplifier. These values are different from the gain and bandwidth of your original amplifier. There are several reasons. The I_d is very sensitive due to the change of ΔV with explicit voltage bias, the ΔV_2 wouldn't adapt all the time, but with use current mirror, I_d is only depends on the ratio of width of M2 and M3. In this part, we ignore the effect of body effect. As we use asymptotic approximation technique, bandwidth is not accurate.

3. Calculate the output resistance of the final amplifier and compare it with the output resistance of the CS amplifier used in Task a of Part 1.

In part 1, $R_{out} = 30k\Omega$ approximately as it mainly depends on $1/g_m$. But in Part2 R_{out} is very large because output connect to the drain of PMOS and NMOS $R_{out} = 284k\Omega$. In next question we explain why we use this topology.

4. How output resistance affect the gain and bandwidth?

In this design, R_{out} is very large because output connect to the drain of PMOS and NMOS. So the dominant pole is set by $R_{out} \cdot C_L$. We got

$$BW = \frac{1}{2\pi R_{OUT} C_L}$$

$$\rightarrow BW \propto \frac{1}{R_{OUT}}$$

Midband gain = $g_m \cdot R_{out}$,

$$\rightarrow \text{midband gain} \propto R_{out}$$

From how output resistance affect the gain and bandwidth, we learned that bandwidth is a trade off of midband gain. From part1 to Part2, we try to get larger gain as bandwidth is reduced. So we are suggested to choose parameters widely.

Appendix:

Here we gave out some designs didn't meet all the design specifications before we got the final design. And we provide some solutions to fix them.

1. When we choose $V_{B1} = 1.2V$ rather than final design $V_{B1} = 1.19V$.

Outputs				
	Name/Signal/Exp	Value	Plot	Save
1	3dB_bandwidth	239.553K	<input checked="" type="checkbox"/>	<input type="checkbox"/>
2	midband_gain	143.29	<input checked="" type="checkbox"/>	<input type="checkbox"/>
3	out_swing	1.96281	<input checked="" type="checkbox"/>	<input type="checkbox"/>
4	out_AC	wave	<input checked="" type="checkbox"/>	<input type="checkbox"/>
5	output	wave	<input checked="" type="checkbox"/>	<input type="checkbox"/>

Output swing is too small.

2. At very beginning, we use explicit voltage bias to bias M2, only change the voltage 200mV lower, we got a very large output swing and everything in a mess. It is because one of transistors is in triode.

Outputs				
	Name/Signal/Exp	Value	Plot	Save
1	3dB_bandwidth	15.7679M	<input checked="" type="checkbox"/>	<input type="checkbox"/>
2	midband_gain	1.94156	<input checked="" type="checkbox"/>	<input type="checkbox"/>
3	out_swing	4.63074	<input checked="" type="checkbox"/>	<input type="checkbox"/>
4	out_AC	wave	<input checked="" type="checkbox"/>	<input type="checkbox"/>
5	output	wave	<input checked="" type="checkbox"/>	<input type="checkbox"/>

I tried to change the value of specs and calculated again. And I found that with same expected I_d , using current mirror can solve this problem. It is because if we use a current mirror, whether a transistor in saturation or not is not depends on V_{bias} anymore, the current is set by I_{bias} .